



**Universidade Federal de Santa Catarina**  
**Centro Tecnológico – CTC**  
**Departamento de Engenharia Elétrica**



# **“EEL7020 – Sistemas Digitais”**

**Prof. Eduardo Augusto Bezerra**


**Eduardo.Bezerra@eel.ufsc.br**

**Florianópolis, março de 2010.**

***Tarefa I: circuito com dois flip-flops e um latch***

Arquivo: lab3\_VHDL.pdf  
parte IV
 
# Tarefa I: Circuito com dois FFs e um latch




## Etapas:

1. Implementar o circuito em VHDL, usando o Quartus II, e realizar a síntese.
2. Utilizar a ferramenta em *Tools -> Netlist Viewers -> Technology Map Viewer*, e examinar o circuito gerado pela síntese.
3. Verificar que o latch é implementado em uma lookup table, e para os flip-flops são aproveitados os flip-flops existentes no FPGA da DE2.
4. Realizar a simulação funcional de acordo com os dados descritos no diagrama de formas de onda do próximo slide.
5. Observar as diferenças no comportamento dos três elementos de armazenamento implementados.

# Tarefa I: Circuito com dois FFs e um latch

 
**Resultado esperado da simulação funcional.**



**Sugestão de implementação VHDL:** criar um componente LATCH e um componente FLIP-FLOP e, na descrição VHDL principal (top), utilizar esses componentes para criar o LATCH e os dois FFs, e realizar o mapeamento dos pinos, conectando os diversos sinais com PORT MAP.

 
# Tarefa I: Sugestão de VHDL

```
library ieee;
use ieee.std_logic_1164.all;
entity D_latch is port (
    C: in std_logic;
    D: in std_logic;
    Q: out std_logic
);
end D_latch;
architecture behv of D_latch is
begin
    process(C, D)
    begin
        if (C = '1') then
            Q <= D;
        end if;
    end process;
end behv;
```



 
# Tarefa I: Sugestão de VHDL

```
library ieee;
use ieee.std_logic_1164.all;
entity D_FF is port (
    CLK: in std_logic;
    D: in std_logic;
    Q: out std_logic
);
end D_FF;
architecture behv of D_FF is
begin
    process(CLK, D)
    begin
        if (CLK'event and CLK = '1') then
            Q <= D;
        end if;
    end process;
end behv;
```


 
# Tarefa I: Sugestão de VHDL

```
library ieee;
use ieee.std_logic_1164.all;
entity D_FFd is port (
    CLK: in std_logic;
    D: in std_logic;
    Q: out std_logic
);
end D_FFd;
architecture behv of D_FFd is
begin
    process(CLK, D)
    begin
        if (CLK'event and CLK = '0') then
            Q <= D;
        end if;
    end process;
end behv;
```



# Tarefa I: Sugestão de VHDL

```
library ieee;
use ieee.std_logic_1164.all;
entity lab7 is
    port (D : IN STD_LOGIC;
          CLK : IN STD_LOGIC;
          QA : OUT STD_LOGIC;
          QB : OUT STD_LOGIC;
          QC : OUT STD_LOGIC
    );
end lab7;

architecture top of lab7 is

    component D_latch
        port (
            C: in std_logic;
            D: in std_logic;
            Q: out std_logic
        );
    end component;
```

```
    component D_FF
        port ( CLK: in std_logic;
              D: in std_logic;
              Q: out std_logic
        );
    end component;
```

```
    component D_FFd
        port ( CLK: in std_logic;
              D: in std_logic;
              Q: out std_logic
        );
    end component;
```


```
begin -- início da architecture
    L0: D_latch port map (CLK, D, QA);
    FS: D_FF port map (CLK, D, QB);
    FD: D_FFd port map (CLK, D, QC);
end top; -- fim da architecture
```



***Tarefa II: display de 7-segmentos com registrador***

Arquivo: lab3\_VHDL.pdf  
parte V

# Tarefa II: Sugestão de circuito

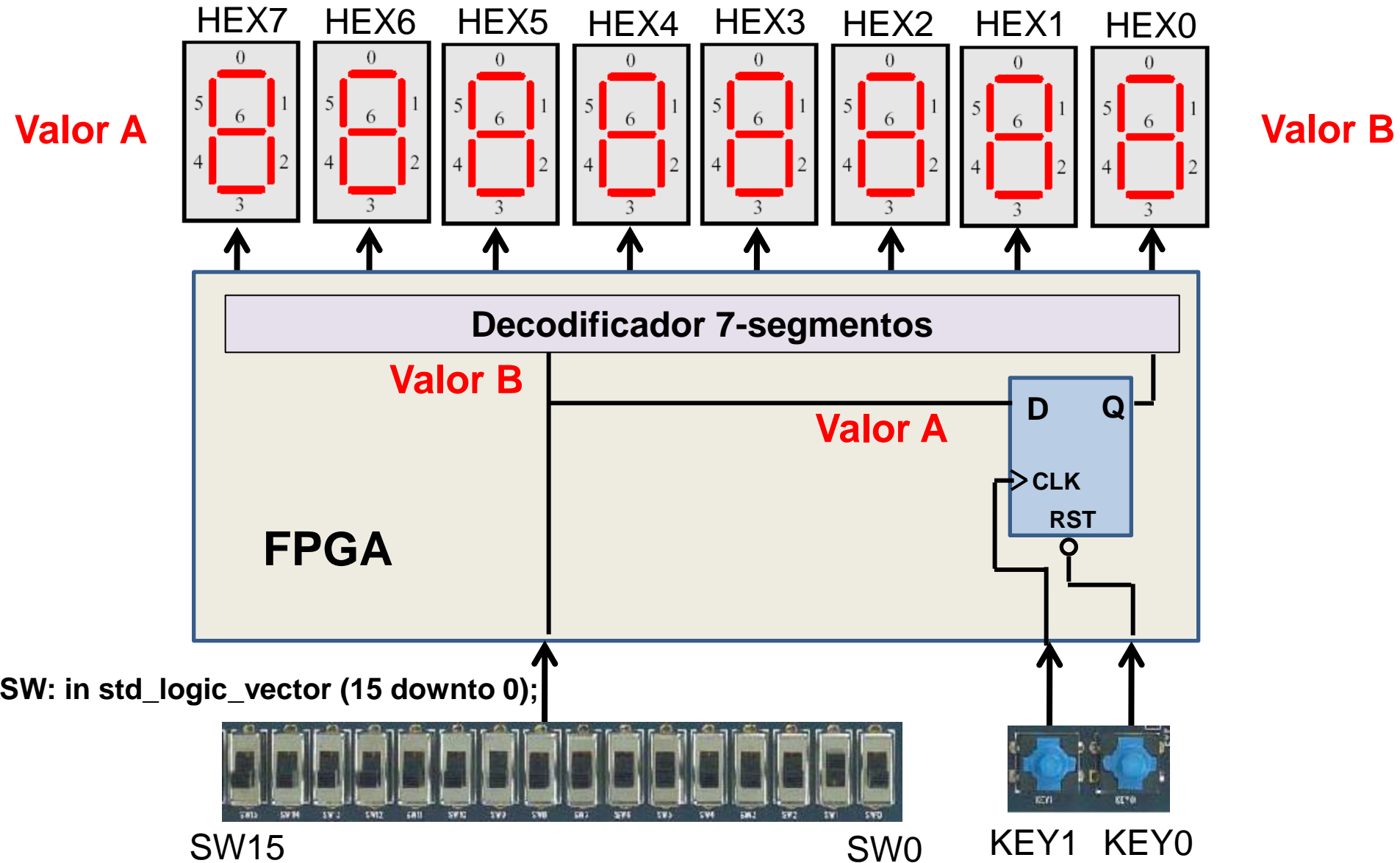

# Tarefa II: Sugestão de VHDL (Prof. Joni Fraga)

---

```
library ieee;
use ieee.std_logic_1164.all;
entity quartus1 is
    port (
        KEY: in std_logic_vector(1 downto 0);
        SW: in std_logic_vector(15 downto 0);
        HEX0 : out std_logic_vector(6 downto 0);
        HEX1 : out std_logic_vector(6 downto 0);
        HEX2 : out std_logic_vector(6 downto 0);
        HEX3 : out std_logic_vector(6 downto 0);
        HEX4 : out std_logic_vector(6 downto 0);
        HEX5 : out std_logic_vector(6 downto 0);
        HEX6 : out std_logic_vector(6 downto 0);
        HEX7 : out std_logic_vector(6 downto 0);
        LEDR: out std_logic_vector(15 downto 0)
    );
end quartus1;
```

# Tarefa II: Sugestão de VHDL (Prof. Joni Fraga)

---

architecture behv of quartus1 is

signal RST, CLK : std\_logic;

signal D, Q : std\_logic\_vector(15 downto 0);

component deco7

port ( d: in std\_logic\_vector(3 downto 0);

f: out std\_logic\_vector(6 downto 0)

);

end component;

begin

D <= SW;

RST <= KEY(0);

CLK <= KEY(1);

DEC0: deco7 port map(Q(3 downto 0),HEX0(6 downto 0));

DEC1: deco7 port map(Q(7 downto 4),HEX1(6 downto 0));

DEC2: deco7 port map(Q(11 downto 8),HEX2(6 downto 0));

DEC3: deco7 port map(Q(15 downto 12),HEX3(6 downto 0));

DEC4: deco7 port map(SW(3 downto 0),HEX4(6 downto 0));

DEC5: deco7 port map(SW(7 downto 4),HEX5(6 downto 0));

DEC6: deco7 port map(SW(11 downto 8),HEX6(6 downto 0));

DEC7: deco7 port map(SW(15 downto 12),HEX7(6 downto 0));

# Tarefa II: Sugestão de VHDL (Prof. Joni Fraga)

---

```
process(CLK, RST, D)
begin
    if (RST = '0') then
        Q <= "000000000000000000";
    elsif (CLK'event and CLK = '1') then
        Q <= D;
    end if;
end process;
end behv;
```

# Tarefa II: Sugestão de VHDL (Prof. Joni Fraga)

```
library ieee;
use ieee.std_logic_1164.all;
-- decodificador 7 segmentos
entity deco7 is
  port (
    d : in std_logic_vector(3 downto 0);
    f : out std_logic_vector(6 downto 0)
  );
end deco7;
```

```
architecture dec_beh of deco7 is
begin
  f <= "1111110" when d="0000" else
        "0110000" when d="0001" else
        "1101101" when d="0010" else
        "1111001" when d="0011" else
        "0110011" when d="0100" else
        "1011011" when d="0101" else
        "1011111" when d="0110" else
        "1110000" when d="0111" else
        "1111111" when d="1000" else
        "1110011" when d="1001" else
        "1110111" when d="1010" else
        "0011111" when d="1011" else
        "1001110" when d="1100" else
        "0111101" when d="1101" else
        "1001111" when d="1110" else
        "1000111";
end dec_beh;
```