



Universidade Federal de Santa Catarina
Centro Tecnológico – CTC
Departamento de Engenharia Elétrica



“EEL7020 – Sistemas Digitais”

Prof. Eduardo Augusto Bezerra

Eduardo.Bezerra@eel.ufsc.br

Florianópolis, agosto de 2011.

Sistemas Digitais

Processos implícitos e explícitos

Processos implícitos e explícitos

Processos implícitos:

- Atribuições com sinais em paralelo (exemplo: `LEDR <= SW`);
- Atribuições com seleção (*with / select*) e comparação (*when*);
- Componentes instanciados (*component / port map*);

Processos explícitos:

- Definidos com a palavra reservada ***process***.

Processos implícitos e explícitos

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY implicito IS
PORT (
    a, b : IN STD_LOGIC;
    y    : OUT STD_LOGIC
);
END implicito;
ARCHITECTURE logic OF implicito IS
    SIGNAL c : STD_LOGIC;
BEGIN
    c <= a AND b;
    y <= c;
END logic;
```

- **Soluções equivalentes;**
- **Exemplo adaptado de material educacional da Altera.**

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY explicito IS
PORT (
    a,b : IN STD_LOGIC;
    y : OUT STD_LOGIC
);
END explicito;
ARCHITECTURE logic OF explicito IS
    SIGNAL c : STD_LOGIC;
BEGIN
    PROCESS (a, b)
    BEGIN
        c <= a AND b;
    END PROCESS;
    PROCESS (c)
    BEGIN
        y <= c;
    END PROCESS;
END logic;
```

Processos implícitos e explícitos

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY implicito IS
PORT (
    a, b : IN STD_LOGIC;
    y    : OUT STD_LOGIC
);
END implicito;
ARCHITECTURE logic OF implicito IS
    SIGNAL c : STD_LOGIC;
BEGIN
    c <= a AND b;
    y <= c;
END logic;
```

- Soluções **NÃO SÃO** equivalentes;
- Exemplo adaptado de material educacional da Altera.


```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY explicito IS
PORT (
    a,b : IN STD_LOGIC;
    y : OUT STD_LOGIC
);
END explicito;
ARCHITECTURE logic OF explicito IS
    SIGNAL c : STD_LOGIC;
BEGIN
    PROCESS (a, b)
    BEGIN
        c <= a AND b;
        y <= c;
    END PROCESS;
END logic;
```

Processos **implícitos** – revisão de atribuição condicional

architecture x of y is
begin

```
q <= a when sela = '1' else  
    b when selb = '1' else  
    c;
```


end x;

 

architecture x of y is
begin

```
with sel select  
q <= a when "00",  
    b when "01",  
    c when "10",  
    d when others;
```

end x;

 


Processos **explícitos** – comparação e seleção

architecture **implicito** of y is
begin

```
q <= a when sela = '1' else  
    b when selb = '1' else  
    c;
```

end implicito;

 

architecture **explicito** of y is
begin

```
process (sela, selb, a, b, c)  
begin
```

```
    if sela='1' then
```

```
        q <= a;
```

```
    elsif selb = '1' then
```

```
        q <= b;
```

```
    else
```

```
        q <= c;
```

```
    end if;
```

```
end process;
```

end explicito;

Processos **explícitos** – comparação e seleção

architecture **implicito** of y is
begin

with sel **select**


q <= a **when** “00”,

b **when** “01”,

c **when** “10”,

d **when** others;

end implicito;

 

architecture **explicito** of y is
begin

process (sel, a, b, c, d)
begin

case sel **is**

when “00” =>

q <= a;

when “01” =>

q <= b;

when “10” =>

q <= c;

when others =>

q <= d;

end case;

end process;

end explicito;

Estudo de caso: uso de processo explícito para implementar registrador com reset assíncrono, clock e sinal de enable

Deslocamento de vetor de entrada 1 bit à esquerda (1/2)

- sr_in recebe palavra de N bits (vetor de N bits). A cada
- pulso de clock, a palavra em sr_in é deslocada 1 bit para a
- esquerda, e copiada para sr_out, também de N bits.

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity desloc_1_bit_esq is
```

```
    generic ( N : natural := 64 );
```

```
    port      ( clk          : in std_logic;
```

```
                enable      : in std_logic;
```

```
                reset       : in std_logic;
```

```
                sr_in       : in std_logic_vector((N - 1) downto 0);
```

```
                sr_out      : out std_logic_vector((N - 1) downto 0)
```

```
            );
```

```
end entity;
```

Deslocamento de vetor de entrada 1 bit à esquerda (2/2)

architecture rtl of desloc_1_bit_esq is

signal sr: std_logic_vector ((N - 1) downto 0); -- Registrador de N bits

begin

process (clk, reset)

begin

if (reset = '0') then -- *Reset assíncrono do registrador*

sr <= (others => '0');

elsif (rising_edge(clk)) then -- *Sinal de clock do registrador (subida)*

if (enable = '1') then -- *Sinal de enable do registrador*

-- Desloca 1 bit para a esquerda. Bit mais significativo é perdido.

sr((N - 1) downto 1) <= sr_in((N - 2) downto 0);

sr(0) <= '0';


end if;

end if;

end process;


sr_out <= sr;

end rtl;

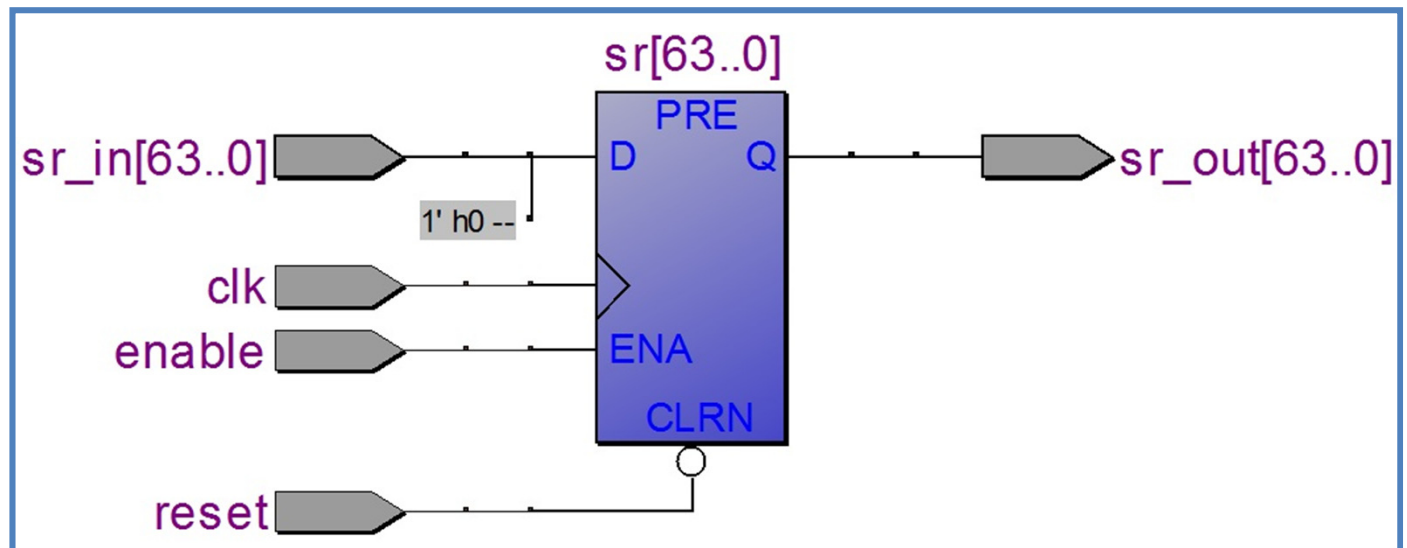

Deslocamento de vetor de entrada 1 bit à esquerda

Valor de entrada em *sr_in* = 93H

 

Valor de saída em *sr_out* = 26H

Tarefa: multiplicação e divisão por 2 na calculadora do Lab. 6


Tarefa – Descrição Textual

- Utilizando **registradores de deslocamento**, incluir no projeto da calculadora do lab. 6, um componente para **multiplicação por 2** e um componente para **divisão por 2**.
- Incluir um **registrador de 8 bits** para armazenar o resultado das operações realizadas (soma, multiplicação e divisão).
- Utilizar as chaves S0 a S7 para entrar com o operando A, e as chaves S8 a S15 para entrar com o operando B.
- Usar as chaves S16 e S17 para selecionar a operação desejada (soma, multiplicação e divisão).
- Sempre que um determinado botão da placa for pressionado (KEY0), o resultado da operação especificada nas chaves S16 e S17 (8 bits) deverá ser armazenado em um registrador de 8 bits.
- O valor contido no registrador de 8 bits deverá estar continuamente sendo apresentado em dois **displays** de 7-segmentos.
- Utilizar decodificadores de binário para 7-segmentos na saída do registrador de armazenamento dos resultados.

Diagrama de blocos de calculadora com somador de 8 bits, multiplicação por 2 e divisão por 2.


EEL7020 – Sistemas Digitais

Prof. Eduardo Bezerra, EEL/UFSC

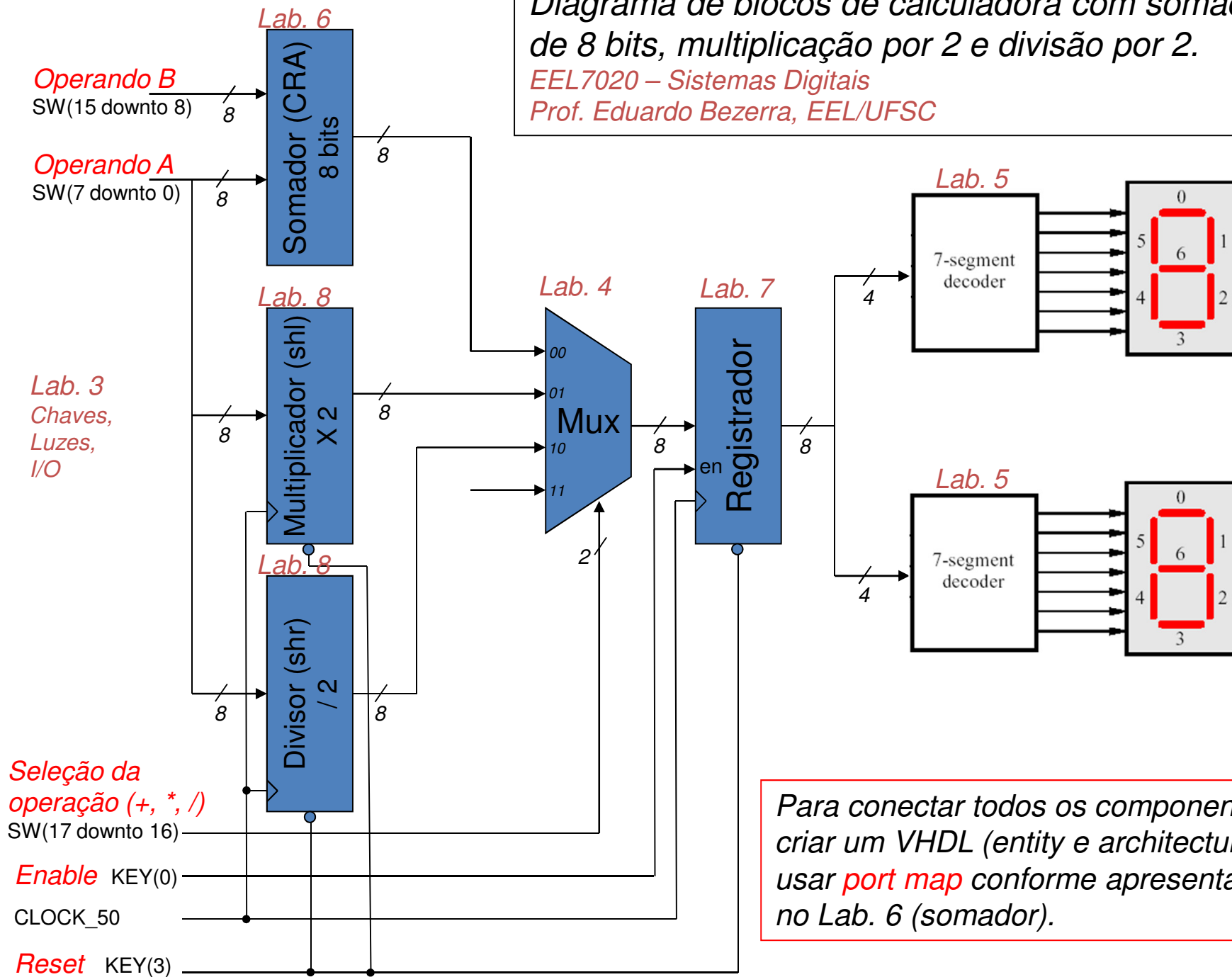

*Para conectar todos os componentes, criar um VHDL (entity e architecture) e usar **port map** conforme apresentado no Lab. 6 (somador).*

Diagrama de blocos gerado pelo *netlist viewer*

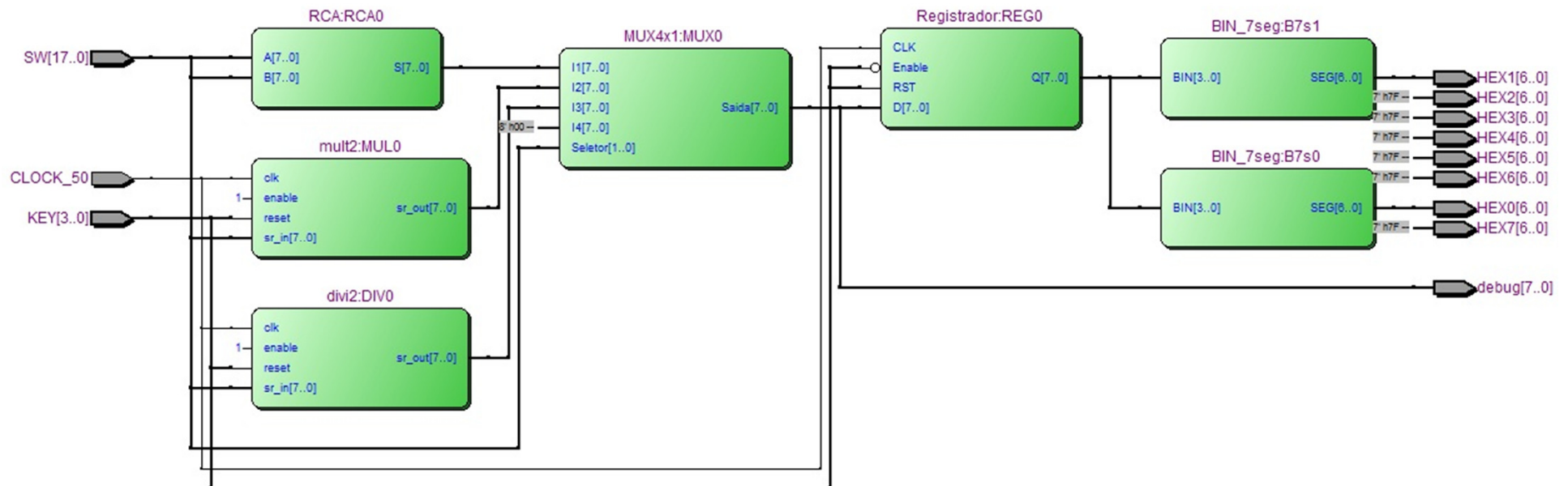

Simulação com *ModelSim*

Simulação do projeto com ModelSim

1. Criar uma nova pasta dentro da pasta do projeto.
2. Copiar os **scripts de simulação** disponíveis na página da disciplina para dentro da nova pasta.
3. Entrar na nova pasta, editar o arquivo "*compila.do*", e alterar **calculadora.vhd** para o nome do seu arquivo VHDL a ser simulado.
4. Copiar APENAS o seu arquivo VHDL (calculadora) a ser simulado para a nova pasta, que já deve possuir os **scripts** de simulação copiados da página da disciplina.
5. Executar o *ModelSim-Altera*, que se encontra no menu *Iniciar* do Windows, pasta "*Altera*".
6. No menu "*File*" do *ModelSim*, definir a pasta do projeto (opção "*Change Directory*"), selecionando a nova pasta.

Simulação do projeto com ModelSim (cont.)

7. Execução da simulação (arquivo *compila.do*)
 - a) No menu "Tools" do ModelSim, selecionar "*Tcl*" -> "*Execute Macro*".
 - b) Selecionar o arquivo "*compila.do*", e "*Open*".
8. O *ModelSim* irá compilar os arquivos VHDL e iniciar a simulação.
9. A janela com as formas de onda irá abrir, apresentando o resultado da simulação.

Obs. Se desejar, editar o arquivo *tb.vhd* para alterar a simulação a ser realizada, e repetir o passo 7.

Simulação do projeto com ModelSim (cont.)

Obs. Se o resultado da simulação não estiver de acordo com o esperado, alterar o seu VHDL, salvar, e executar novamente a simulação (arquivo *compila.do*).

Obs. A simulação só irá funcionar se o seu projeto possuir EXATAMENTE a seguinte *entity*:

```
entity Calculadora is
```

```
    port ( SW : IN STD_LOGIC_VECTOR(17 downto 0);
```

```
          KEY : IN STD_LOGIC_VECTOR(3 downto 0);
```

```
          HEX0 : OUT STD_LOGIC_VECTOR(6 downto 0);
```

```
    ...
```

```
          HEX7 : OUT STD_LOGIC_VECTOR(6 downto 0);
```

```
          debug: OUT STD_LOGIC_VECTOR(7 downto 0));
```

```
end Calculadora;
```




Simulação do projeto com ModelSim (cont.)

Obs. O arquivo "*compila.do*" contém os comandos do *ModelSim* necessários para realizar a simulação, incluindo:

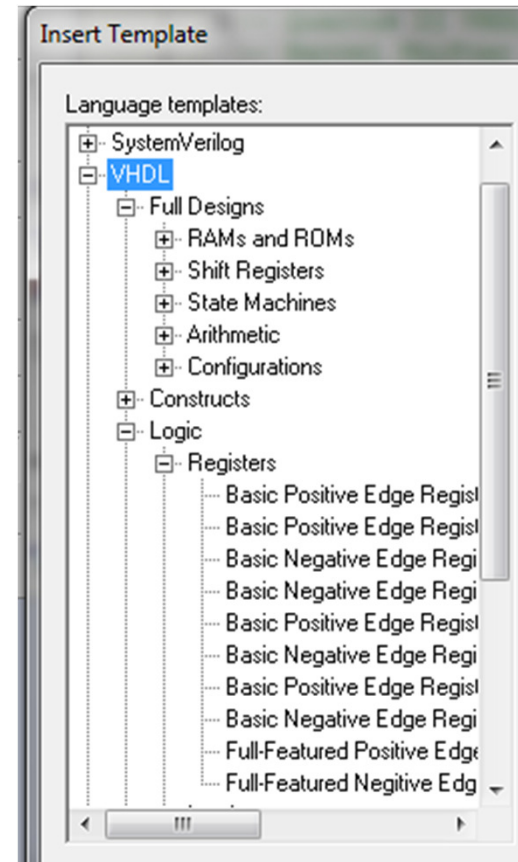 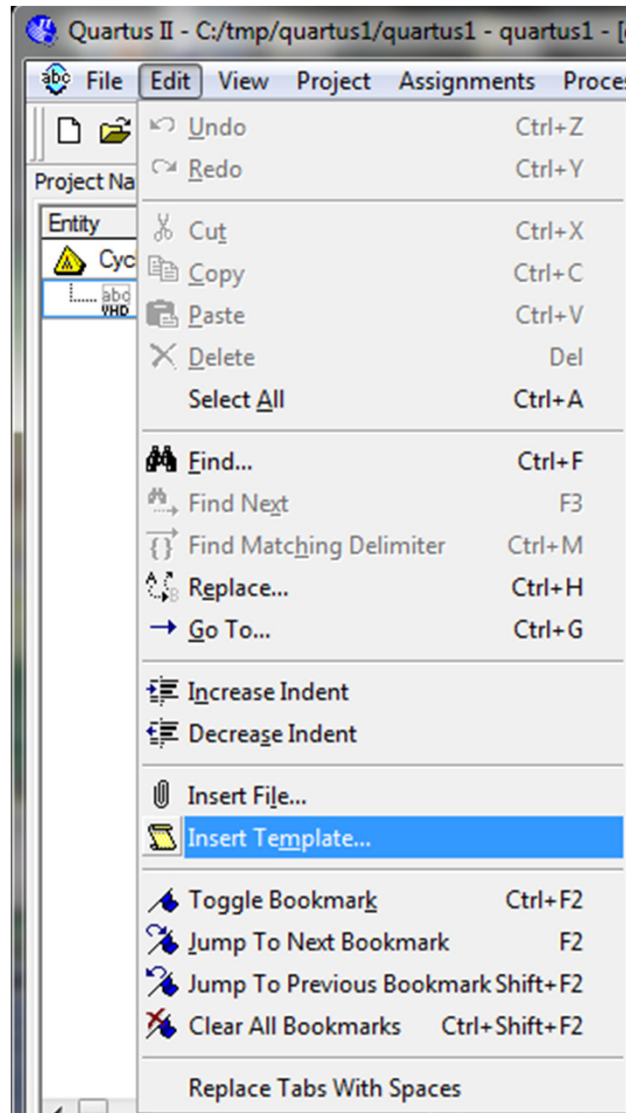- a) Criação da biblioteca de trabalho - comando *vlib*.
- b) Compilação dos arquivos VHDL para a biblioteca de trabalho - comando *vcom*.
- c) Inicialização do simulador com o arquivo *testbench* - comando *vsim*.
- d) Execução da janela de formas de onda (*waveform*) - comando *wave*.
- e) Adição dos sinais na janela de formas de onda - comando *wave*.
- f) Execução da simulação - comando *run*.

***Outros templates com
processos explícitos do Quartus II***

Quartus II – Templates de descrições VHDL com processos



Basic Positive Edge Register with Asynchronous Reset and Clock Enable

```
process (<clock_signal>, <reset>)
begin
    -- Reset whenever the reset signal goes low, regardless
    -- of the clock or the clock enable
    if (<reset> = '0') then
        <register_variable> <= '0';
        -- If not resetting, and the clock signal is enabled,
        -- update the register output on the clock's rising edge
    elsif (rising_edge(<clock_signal>)) then
        if (<clock_enable> = '1') then
            <register_variable> <= <data>;
        end if;
    end if;
end process;
```


Basic Positive Edge Register with Asynchronous Reset

```
process (CLK, RST)
begin
```

```
-- Reset whenever the reset signal goes low, regardless
-- of the clock
```

```
if (RST = '0') then
```

```
    Q <= '0';
```

```
-- If not resetting update the register output
```


```
-- on the clock's rising edge
```

```
elsif (CLK'event and CLK = '1') then
```

```
    Q <= D;
```

```
end if;
```

```
end process;
```

 

Binary counter (1/2)

-- Binary counter

library ieee;

use ieee.std_logic_1164.all;

use ieee.numeric_std.all;

entity binary_counter is

 generic (MIN_COUNT : natural := 0;
 MAX_COUNT : natural := 255);

 port (

 clk : in std_logic;

 reset : in std_logic;

 enable : in std_logic;

 q: out integer range MIN_COUNT to MAX_COUNT
);

end entity;

Binary counter (2/2)

```
architecture rtl of binary_cunter is
begin
    process (clk)
        variable cnt: integer range MIN_COUNT to MAX_COUNT;
    begin
        if (rising_edge(clk)) then
            if (reset = '1') then
                -- Reset counter to 0
                cnt := 0;
            elsif enable = '1' then
                cnt := cnt + 1;
            end if;
        end if;
        -- Output the current count
        q <= cnt;
    end process;
end rtl;
```

Basic Shift Register with Asynchronous Reset (1/2)

-- One-bit wide, N-bit long shift register with asynchronous reset

library ieee;

use ieee.std_logic_1164.all;

entity basic_shift_register_asynchronous_reset is

generic (NUM_STAGES : natural := 256);

port (clk : in std_logic;
enable : in std_logic;
reset : in std_logic;
sr_in : in std_logic;
sr_out : out std_logic
);

end entity;

Basic Shift Register with Asynchronous Reset (2/2)

```
architecture rtl of basic_shift_register_asynchronous_reset is
    type sr_length is array ((NUM_STAGES-1) downto 0) of std_logic;
    signal sr: sr_length;           -- Declare the shift register
begin
    process (clk, reset)
    begin
        if (reset = '1') then
            sr <= (others => '0');
        elsif (rising_edge(clk)) then
            if (enable = '1') then
                -- Shift data by one stage; data from last stage is lost
                sr((NUM_STAGES-1) downto 1) <= sr((NUM_STAGES-2) downto 0);
                sr(0) <= sr_in;
            end if;
        end if;
    end process;
    sr_out <= sr(NUM_STAGES-1);
end rtl;
```

Four-State Mealy State Machine (1/5)

- A Mealy machine has outputs that depend on both the state and the
- inputs. When the inputs change, the outputs are updated immediately,
- without waiting for a clock edge. The outputs can be written more than
- once per state or per clock cycle.

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity four_state_mealy_state_machine is
```

```
port (
```

```
    clk      : in std_logic;
```

```
    input    : in std_logic;
```

```
    reset    : in std_logic;
```

```
    output   : out std_logic_vector (1 downto 0)
```

```
);
```

```
end entity;
```

Four-State Mealy State Machine (2/5)

```
architecture rtl of four_state_mealy_state_machine is
    -- Build an enumerated type for the state machine
    type state_type is (s0, s1, s2, s3);
    signal state : state_type;      -- Register to hold the current state
begin
    process (clk, reset)
    begin
        if (reset = '1') then
            state <= s0;
        elsif (rising_edge(clk)) then
            -- Determine the next state synchronously, based on
            -- the current state and the input
            case state is
                when s0 =>
                    if input = '1' then state <= s1;
                    else state <= s0;
                    end if;
            end case;
        end if;
    end process;
end;
```

Four-State Mealy State Machine (3/5)

```
when s1 =>
    if input = '1' then state <= s2;
    else                state <= s1;
    end if;
when s2 =>
    if input = '1' then state <= s3;
    else                state <= s2;
    end if;
when s3 =>
    if input = '1' then state <= s3;
    else                state <= s1;
    end if;
end case;
end if;
end process;
```


Four-State Mealy State Machine (4/5)

- Determine the output based only on the current state
- and the input (do not wait for a clock edge).

```
process (state, input)
begin
    case state is
        when s0 =>
            if input = '1' then
                output <= "00";
            else
                output <= "01";
            end if;
```

Four-State Mealy State Machine (5/5)

```
when s1 =>
    if input = '1' then output <= "01";
    else                output <= "11";
    end if;
when s2 =>
    if input = '1' then output <= "10";
    else                output <= "10";
    end if;
when s3 =>
    if input = '1' then output <= "11";
    else                output <= "10";
    end if;
end case;
end process;
end rtl;
```

Four-State Moore State Machine (1/4)

- A Moore machine's outputs are dependent only on the current state.
- The output is written only when the state changes. (State
- transitions are synchronous.)

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity four_state_moore_state_machine is
```

```
port (
```

```
    clk      : in std_logic;
```

```
    input    : in std_logic;
```

```
    reset    : in std_logic;
```

```
    output   : out std_logic_vector (1 downto 0)
```

```
);
```

```
end entity;
```

Four-State Moore State Machine (2/4)

```
architecture rtl of four_state_moore_state_machine is
    -- Build an enumerated type for the state machine
    type state_type is (s0, s1, s2, s3);
    signal state : state_type;      -- Register to hold the current state
begin
    process (clk, reset)
    begin
        if (reset = '1') then
            state <= s0;
        elsif (rising_edge(clk)) then
            -- Determine the next state synchronously, based on
            -- the current state and the input
            case state is
                when s0 =>
                    if input = '1' then state <= s1;
                    else state <= s0;
                    end if;
            end case;
        end if;
    end process;
end;
```

Four-State Moore State Machine (3/4)

```
when s1 =>
    if input = '1' then state <= s2;
    else                state <= s1;
    end if;
when s2 =>
    if input = '1' then state <= s3;
    else                state <= s2;
    end if;
when s3 =>
    if input = '1' then state <= s3;
    else                state <= s1;
    end if;
end case;
end if;
end process;
```

Four-State Moore State Machine (4/4)

-- Output depends solely on the current state.

```
process (state, input)
begin
    case state is
        when s0 =>
            output <= "00";
        when s1 =>
            output <= "01";
        when s2 =>
            output <= "10";
        when s3 =>
            output <= "11";
    end case;
end process;
end rtl;
```

Single-port RAM with initial contents (1/4)

-- Single-port RAM with single read/write address and initial contents

library ieee;

use ieee.std_logic_1164.all;

use ieee.numeric_std.all ;

entity single_port_ram_with_init is

generic (DATA_WIDTH : natural := 8;
 ADDR_WIDTH : natural := 6);

port (

 clk : in std_logic;

 addr: in natural range 0 to 2**ADDR_WIDTH - 1;

 data: in std_logic_vector((DATA_WIDTH-1) downto 0);

 we : in std_logic := '1';

 q : out std_logic_vector((DATA_WIDTH -1) downto 0)
);

end single_port_ram_with_init;

Single-port RAM with initial contents (2/4)

architecture rtl **of** single_port_ram_with_init **is**

-- Build a 2-D array type for the RAM

subtype word_t is std_logic_vector((DATA_WIDTH-1) downto 0);
type memory_t is array(2**ADDR_WIDTH-1 downto 0) of word_t;

function init_ram return memory_t is

 variable tmp : memory_t := (others => (others => '0'));

begin

 for addr_pos in 0 to 2**ADDR_WIDTH - 1 loop

 -- Initialize each address with the address itself

 tmp(addr_pos) := std_logic_vector(to_unsigned(addr_pos,
 DATA_WIDTH));

 end loop;

 return tmp;

end init_ram;

Single-port RAM with initial contents (3/4)

- Declare the RAM signal and specify a default value.
- Quartus II will create a memory initialization file (.mif) based on
- the default value.

```
signal ram : memory_t := init_ram;
```

- Register to hold the address

```
signal addr_reg : natural range 0 to 2**ADDR_WIDTH-1;
```

Single-port RAM with initial contents (4/4)

```
begin
    process(clk)
    begin
        if (rising_edge(clk)) then
            if (we = '1') then
                ram(addr) <= data;
            end if;
            -- Register the address for reading
            addr_reg <= addr;
        end if;
    end process;
    q <= ram(addr_reg);
end rtl;
```