



Universidade Federal de Santa Catarina
Centro Tecnológico – CTC
Departamento de Engenharia Elétrica



“EEL7020 – Sistemas Digitais”

Prof. Eduardo Augusto Bezerra

Eduardo.Bezerra@eel.ufsc.br


Florianópolis, março de 2010.

Sistemas Digitais

*Projeto de somador de 8 bits
“construindo uma calculadora”*


Arquivo: lab2_VHDL.pdf
parte III

Projeto de somador de 4 bits

 

b	a	c_i	c_o	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

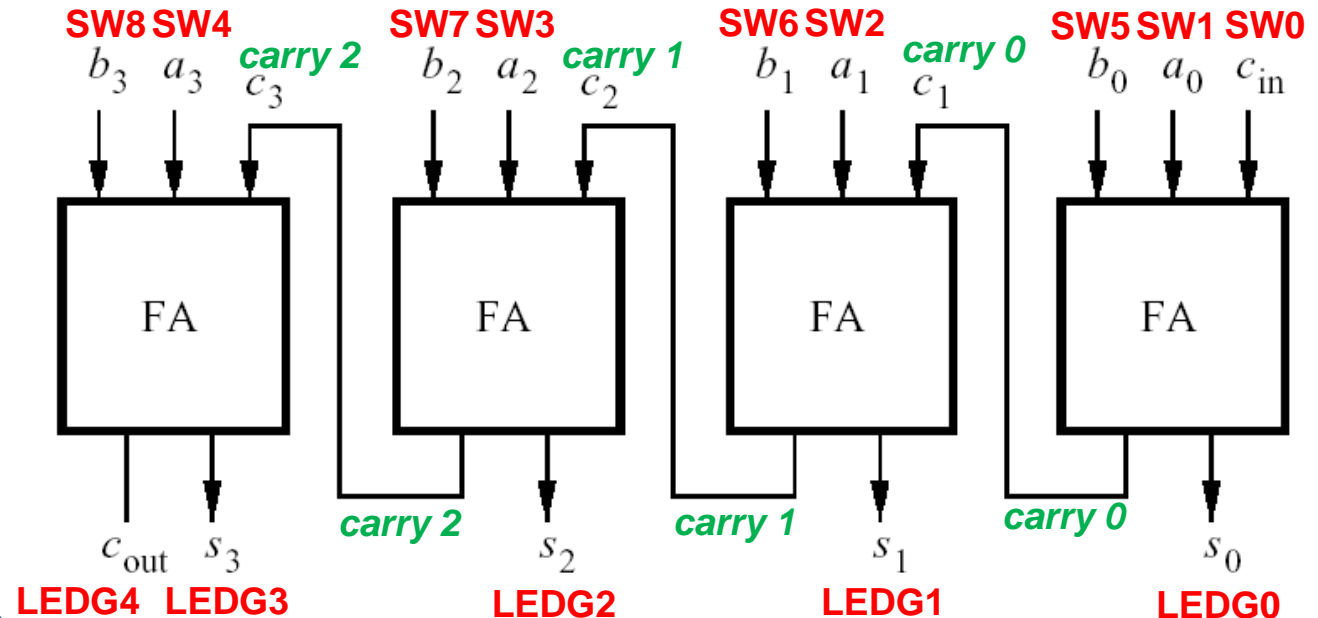Ripple-carry adder de 4 bits, construído com 4 FAs



Tarefas

A partir da Solução II apresentada anteriormente, implementar um somador de 8 bits com as seguintes entradas e saídas:

Entrada Cin e A

SW(0) = Cin
 SW(1) = A0
 SW(2) = A1
 SW(3) = A2
 SW(4) = A3
 SW(5) = A4
 SW(6) = A5
 SW(7) = A6
 SW(8) = A7

Entrada B

SW(9) = B0
 SW(10) = B1
 SW(11) = B2
 SW(12) = B3
 SW(13) = B4
 SW(14) = B5
 SW(15) = B6
 SW(16) = B7

Saída Soma

LEDG(0) = S0
 LEDG(1) = S1
 LEDG(2) = S2
 LEDG(3) = S3
 LEDG(4) = S4
 LEDG(5) = S5
 LEDG(6) = S6
 LEDG(7) = S7

Saída Flags

LEDR(0) = carry out
 LEDR(1) = overflow
 LEDR(2) = negativo
 LEDR(3) = zero

	C ₈	C ₇	C ₆	C ₅	C ₄	C ₃	C ₂	C ₁	←	"vai-um" (<i>carry</i>)	
		A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀	←	1° operando
+		B ₇	B ₆	B ₅	B ₄	B ₃	B ₂	B ₁	B ₀	←	2° operando
		S ₇	S ₆	S ₅	S ₄	S ₃	S ₂	S ₁	S ₀	←	soma

```

library ieee;
use ieee.std_logic_1164.all;
-- somador completo (FA)
entity FA is
  port (a, b, c: in std_logic;
        soma, carry: out std_logic);
end FA;
architecture FA_beh of FA is
begin
  soma <= (a xor b) xor c;
  carry <= b when ((a xor b) = '0')
            else c;
end FA_beh;

```

```

SW(1) = A0
SW(2) = A1
SW(3) = A2
SW(4) = A3
SW(5) = A4
SW(6) = A5
SW(7) = A6
SW(8) = A7

```

```

SW(9) = B0
SW(10) = B1
SW(11) = B2
SW(12) = B3
SW(13) = B4
SW(14) = B5
SW(15) = B6
SW(16) = B7

```

```

LEDG(0) = S0
LEDG(1) = S1
LEDG(2) = S2
LEDG(3) = S3
LEDG(4) = S4
LEDG(5) = S5
LEDG(6) = S6
LEDG(7) = S7

```

```
SW(0) = Cin
```

```

LEDR(0) = carry out
LEDR(1) = overflow
LEDR(2) = negativo
LEDR(3) = zero

```

```

library ieee;
use ieee.std_logic_1164.all;
entity RCA is
  port (SW : IN STD_LOGIC_VECTOR(17 downto 0);
        LEDG : OUT STD_LOGIC_VECTOR(7 downto 0) ;
        LEDR : OUT STD_LOGIC_VECTOR(17 downto 0)
        );
end RCA;
architecture RCA_stru of RCA is
  signal c: std_logic_vector (7 downto 0);
  signal s: std_logic_vector (7 downto 0);
  component FA
    port (a, b, c: in std_logic;
          soma, carry: out std_logic);
  end component;
begin
  FA0: FA port map (sw(1), sw(9), sw(0), s(0), c(0));
  FA1: FA port map (sw(2), sw(10), c(0), s(1), c(1));
  FA2: FA port map (sw(3), sw(11), c(1), s(2), c(2));
  FA3: FA port map (sw(4), sw(12), c(2), s(3), c(3));
  FA4: FA port map (sw(5), sw(13), c(3), s(4), c(4));
  FA5: FA port map (sw(6), sw(14), c(4), s(5), c(5));
  FA6: FA port map (sw(7), sw(15), c(5), s(6), c(6));
  FA7: FA port map (sw(8), sw(16), c(6), s(7), c(7));
  LEDG <= s;
  LEDR(0) <= c(7);           -- carry out
  LEDR(1) <= c(6) xor c(7);  -- overflow
  LEDR(2) <= s(7);          -- negativo
  LEDR(3) <= '1' when (s = "00000000") else '0';  -- zero
end RCA_stru;

```