



**Universidade Federal de Santa Catarina**  
**Centro Tecnológico – CTC**  
**Departamento de Engenharia Elétrica**



# **“EEL7020 – Sistemas Digitais”**

**Prof. Eduardo Augusto Bezerra**


**Eduardo.Bezerra@eel.ufsc.br**

**Florianópolis, agosto de 2011.**

## ***Projeto de multiplexador 2 x 1 de 8 bits***
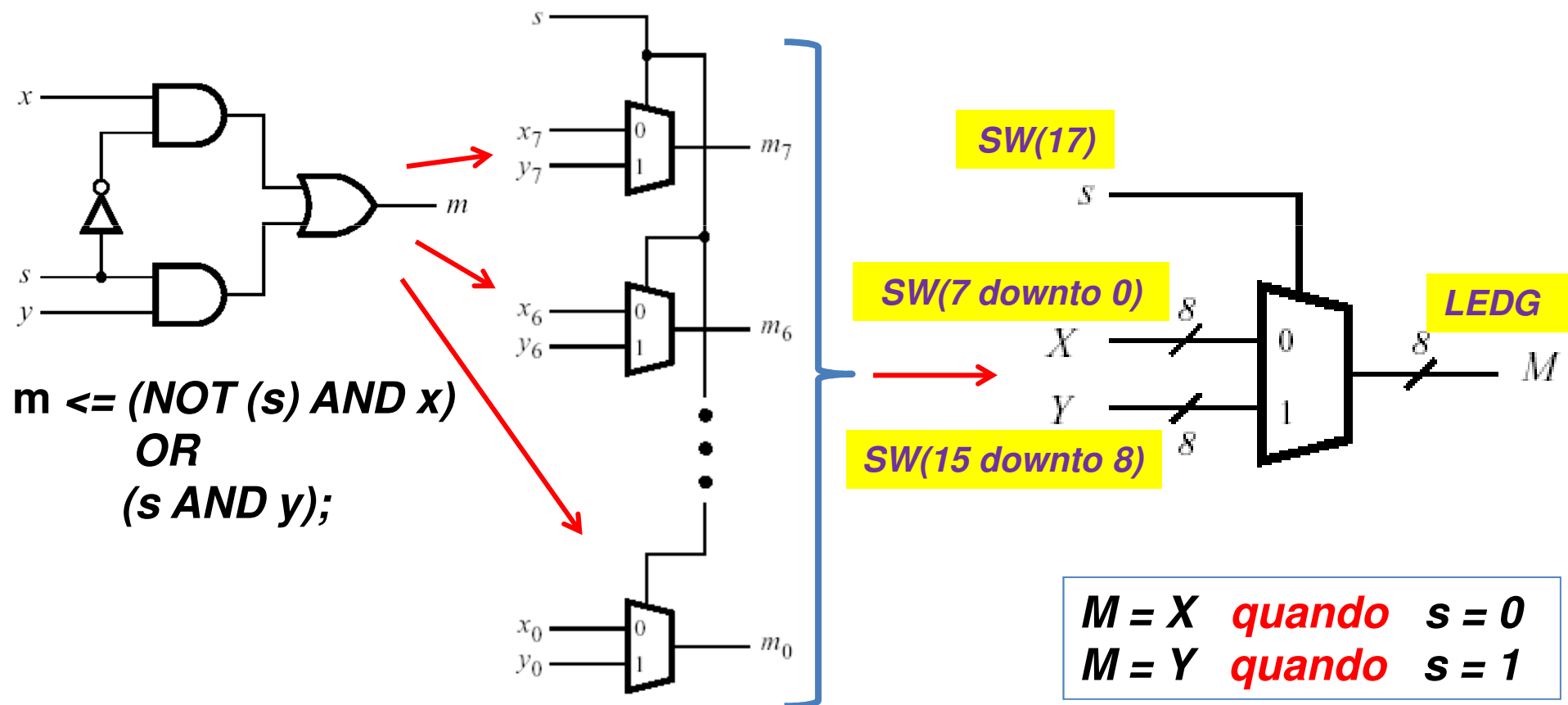
# Projeto de multiplexador

Projetar um circuito em VHDL com duas entradas de 8 bits, X e Y, e produzir uma saída M de 8 bits. Se  $s = 0$ ,  $M = X$ . Se  $S = 1$ ,  $M = Y$ .



## PARTE I


```

library ieee;
use ieee.std_logic_1164.all;

entity part1 is
    port (
        SW    : in std_logic_vector(17 downto 0);
        LEDR  : out std_logic_vector(17 downto 0);
        LEDG  : out std_logic_vector(7 downto 0)
    );
end part1;

architecture behavior of part1 is
begin
    M          S          X          S          Y
    LEDG(0) <= (NOT SW(17) AND SW(15)) OR (SW(17) AND SW(7));
    LEDG(1) <= (NOT SW(17) AND SW(14)) OR (SW(17) AND SW(6));
    LEDG(2) <= (NOT SW(17) AND SW(13)) OR (SW(17) AND SW(5));
    LEDG(3) <= (NOT SW(17) AND SW(12)) OR (SW(17) AND SW(4));
    LEDG(4) <= (NOT SW(17) AND SW(11)) OR (SW(17) AND SW(3));
    LEDG(5) <= (NOT SW(17) AND SW(10)) OR (SW(17) AND SW(2));
    LEDG(6) <= (NOT SW(17) AND SW(9))  OR (SW(17) AND SW(1));
    LEDG(7) <= (NOT SW(17) AND SW(8))  OR (SW(17) AND SW(0));
    LEDR <= SW;
end behavior;

```

 

**$m \leftarrow (\text{NOT } (s) \text{ AND } x) \text{ OR } (s \text{ AND } y);$**

## PARTE II

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity part1 is
```

```
    port ( SW    : in std_logic_vector(17 downto 0);
           LEDR  : out std_logic_vector(17 downto 0);
           LEDG  : out std_logic_vector(7 downto 0)
         );
```

```
end part1;
```

```
architecture behavior of part1 is
```

```
begin
```

```
    LEDG <= SW(7 downto 0) WHEN SW(17) = '1' ELSE SW(15 downto 8);
```

```
    LEDR <= SW;
```


```
end behavior;
```

$S = SW(17)$

$X = SW(7 \text{ downto } 0)$

$Y = SW(15 \text{ downto } 8)$

$M = LEDG$

 

## Tarefa Adicional

```
library ieee;
use ieee.std_logic_1164.all;
entity part2 is
    port ( SW      : in std_logic_vector(1 downto 0);
          LEDR : out std_logic_vector(15 downto 0);
          LEDG : out std_logic_vector(7 downto 0)
        );
end part2;
architecture behavior of part2 is
begin

    LEDG <= "00001111" WHEN SW = "00" ELSE
            "11110000" WHEN SW = "01" ELSE "00000000";
    LEDR <= x"5555" WHEN SW = "10" ELSE
            x"1111"  WHEN SW = "11" ELSE
            x"0000" ;

end behavior;
```